



#/28 RLC Series
LARGE MANY PICS.


Series RCL LAB #28 Greg Moore 2015



Resistor voltage out of phase with source voltage

Series RCL Circuit Analysis & AC Power

28

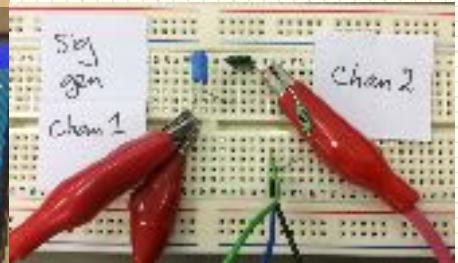

50 kHz Resistor Voltage in phase with source voltage



MEASURE		
V _R	∠	V _L
1.7	43°	
2.34	68°	
2.13	315°	

Resistor Voltage out of phase with source voltage.



Phase angle
@ 100kHz
 25°

100.000

$760 \text{ ns} = 3 \times (1 - 1000)$
0.076

Ans: 360
27.36


Vs leading V_R when the circuit is inductive.


Phase angle @
50kHz

-11°

50.0000

2

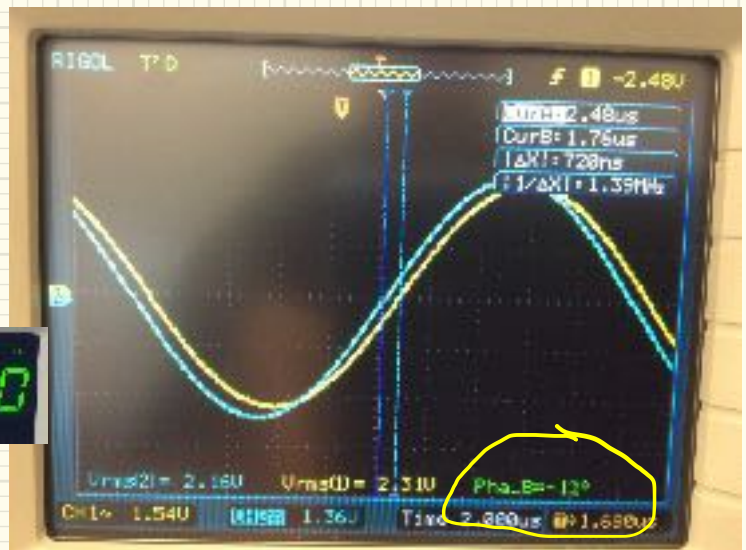

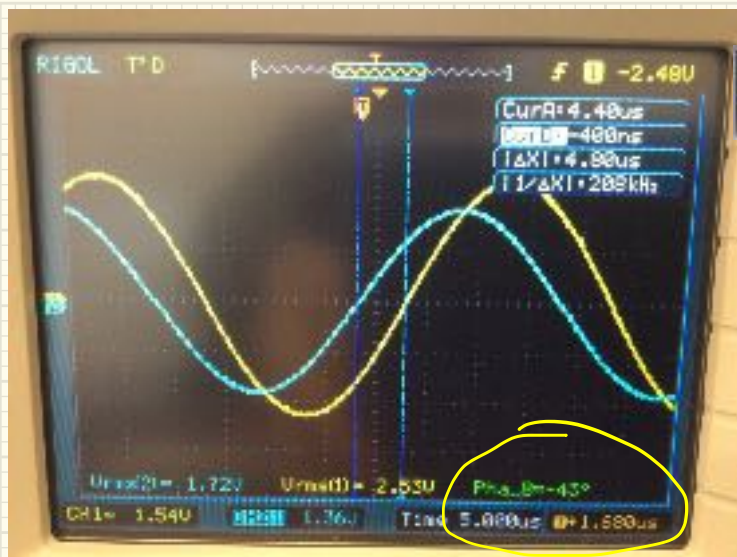


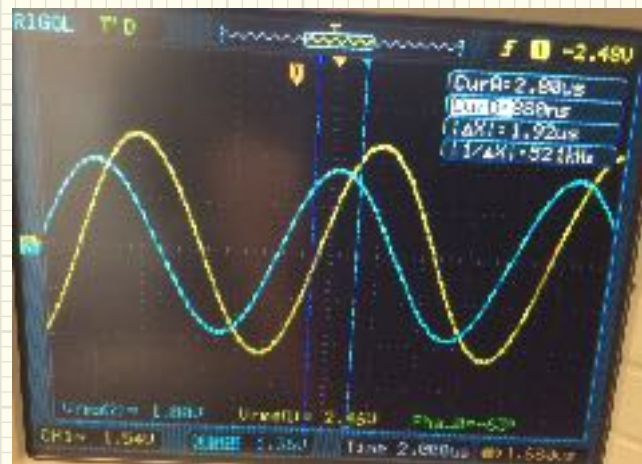25.0000

Phase angle @
25KHz
-43°
V_L leading V_s
here.




circuit rewired to put
inductor in parallel for
V_L measurements.




1000000

V_L @
100 KHz
1.8V_{rms}

3

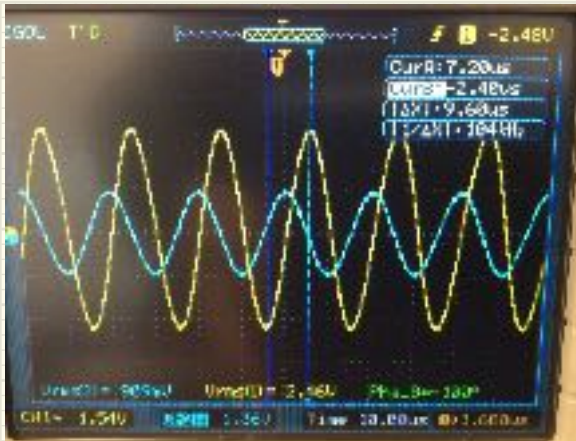

$V_L @ 25KHz$
909mV_{rms}

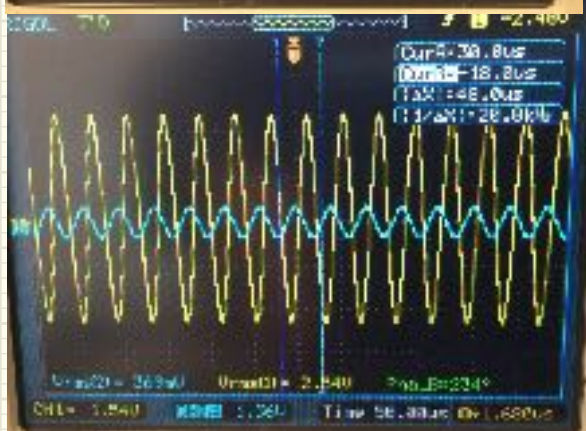


$V_L @ 50KHz$
369mV_{rms}

EXPERIMENTAL									
L	MEASURED					CALC.			
	7	8	9	10		11	12		
ϕ	V_R	ϕ	V_L	V_C		I_L	Z_L	$Z_T = \frac{V_R}{I_T}$ $0.471 \angle \theta$ $I(\text{measured})$	
	1.77	-43°	0.37			3.16	781 Ω		
	2.34	-11°	0.91			4.17	592 Ω		
	2.19	25°	1.8			3.91	631 Ω		



$I_T = \frac{V_R}{R} \rightarrow \frac{V_R(\text{measured})}{560 \Omega}$

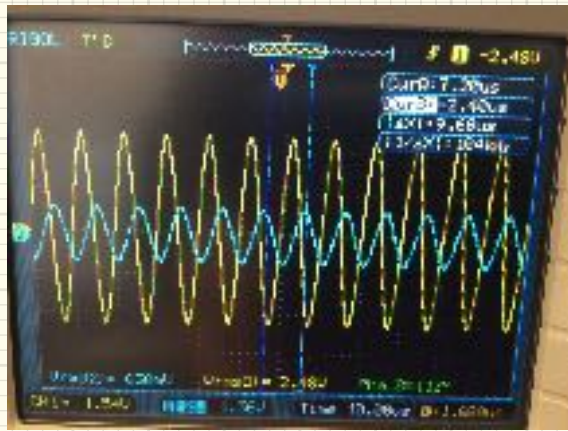Maintain a neat log of the results in the table.



Circuit rewired 3rd time
Cap in parallel.


$V_c @ 100K$
630mV

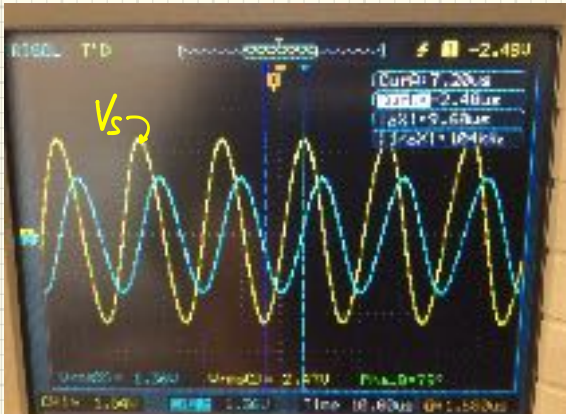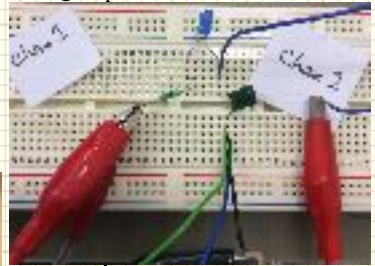

V_s

$V_c @ 50K$
1.36V_{Rms}

Capacitor Voltage lagging
 V_s

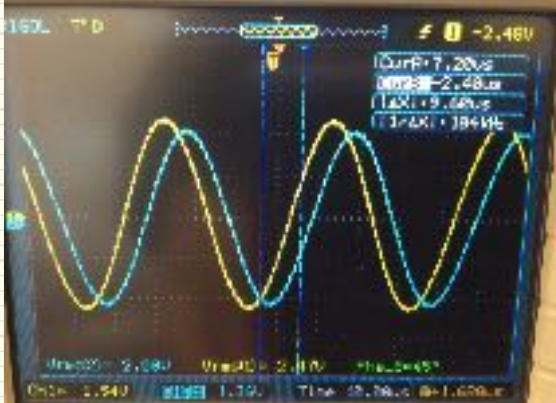

$V_c @ 25K$
2V_{Rms}.

5

PART ONE: SERIES RCL AC CIRCUIT ANALYSIS $(X_C - X_L)^2$

$$X_L = 2\pi fL \quad X_C = 1/(2\pi fC) \quad Z_T = \sqrt{R^2 + (X_L - X_C)^2} \quad I_T = E_S/Z_T$$

$$V_R = R \cdot I_T \quad V_L = X_L \cdot I_T \quad V_C = X_C \cdot I_T \quad \angle \theta = \tan^{-1} [(X_L - X_C)/R]$$

In this part of the experiment, you will analyze a series RCL AC circuit. Your analysis will be theoretical, using formulas only, then experimental, combining circuit measurements and formulas. You will see the same circuit acting inductively at a frequency where $X_L > X_C$, resistively at a frequency where $X_L = X_C$, and capacitively at a frequency where $X_C > X_L$. You will discover that how a circuit acts depends upon component values and the frequency of the source voltage.



- Take a few minutes to mathematically analyze the circuit shown in Figure 1 at the three different frequencies (25 kHz, 50 kHz, and 100 kHz). Use the RMS value of the source voltage for your calculations. Record your answers for total impedance, total current, resistor voltage, inductor voltage, capacitor voltage and angle theta in Table 1. Calculate the inductive and capacitive reactance at the different frequencies and record them here.

0.8 mH $X_L @ 25 \text{ kHz} = 12.56 \Omega$ $X_L @ 50 \text{ kHz} = 25.12 \Omega$ $X_L @ 100 \text{ kHz} = 50.24 \Omega$
 0.01 μF $X_C @ 25 \text{ kHz} = 632.9 \Omega$ $X_C @ 50 \text{ kHz} = 316.2 \Omega$ $X_C @ 100 \text{ kHz} = 159.1 \Omega$

- Assemble the circuit shown in Figure 1a. Apply the first sine wave frequency (25 kHz) at an amplitude of 2 V_{pp}. Set the oscilloscope to trigger on CH-1 (AUTO). CH-1 and CH-2 input mode select should be set to AC. Select a TIME/DIV setting that will display about two cycles on the screen.

2B - Series RCL Circuit Analysis & AC Power

NAME: _____ CLASS: _____ DATE: _____

2.47 V_{pp} = TABLE 1

f	THEORETICAL						EXPERIMENTAL					
	1 Z _T	2 I _T	3 V _R	4 V _L	5 V _C	6 ∠θ	7 V _R	8 ∠θ	9 V _L	10 V _C	11 I _T	12 Z _T
25 kHz	756	3.26 mA	1.92 V	4.00 V	2.00 V	42.3°	1.77 V	-43°	0.317 V	2.00 V	3.16 mA	781 Ω
50 kHz	503	4.81 mA	2.45 V	1.09 V	1.79 V	6.5°	2.34 V	-11°	0.91 V	1.36 V	4.17 mA	592 Ω
100 kHz	656	3.26 mA	2.10 V	1.28 V	0.377 V	31.5°	2.19 V	25°	1.80 V	0.63 V	3.91 mA	631 Ω


$$\sqrt{560^2 + (316 - 251)^2} = 677$$

$$I_T = \frac{V_R}{R} = \frac{V_C(\text{measured})}{X_C} = \frac{560 \Omega}{316 \Omega} = 1.77 \text{ mA}$$

PART ONE QUESTIONS

- At which frequency does the circuit act capacitively? Explain why.


6

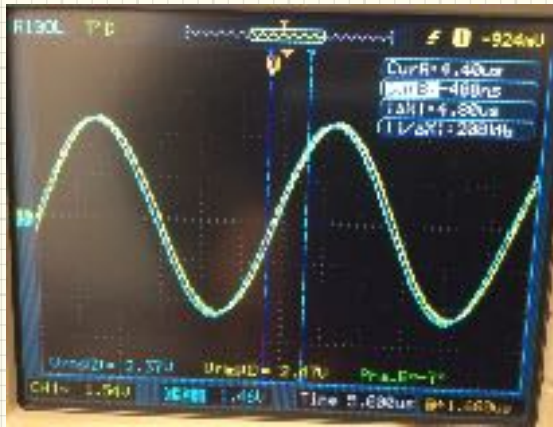

Two capacitors as per Lab guide to improve phase angle & power factor.

350000

per page 170 step 6 + 7

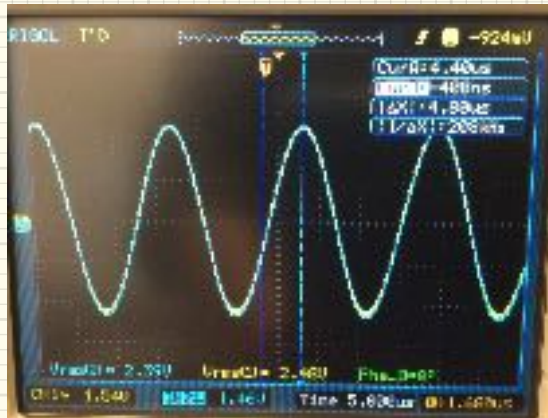

620000

One capacitor with freq increased to give 0° phase shift.



430000

two 0.01 μ F in parallel & 43 kHz for 0° phase shift

7

$$\sqrt{560^2 + (318 - 251)^2} = 67$$

$$I_T = \frac{V_T}{R} \Rightarrow \frac{V_R(\text{measured})}{560\Omega}$$

PART ONE QUESTIONS

- At which frequency does the circuit act capacitively? 25 KHz because $X_C > X_L$ Explain why.
- At which frequency does the circuit act inductively? 100 KHz because $X_L > X_C$ Explain why.
- At which frequency does the circuit act resistively? 50 KHz because $X_C \neq X_L$ begin to equal & cancel out. Explain why.
- When the circuit is acting inductively, what is the amount of effective inductive reactance in the circuit? $X_{L(\text{effective})} = X_L - X_C = 502 - 159 = 343\Omega$
- When the circuit is acting capacitively, what is the amount of effective capacitive reactance in the circuit? $X_{C(\text{effective})} = X_C - X_L = 634 - 125 = 509\Omega$
- List at least three factors that determine how a series RCL circuit will act.
 - frequency
 - choice of components
 - which component is in phase with the other.
- At which frequency was the resistor voltage in phase with the source voltage? 50 KHz
- At any given frequency, what condition must exist in order for the resistor voltage to be in phase with the source voltage applied to a series RCL circuit? Should be no inductive or capacitive effect.

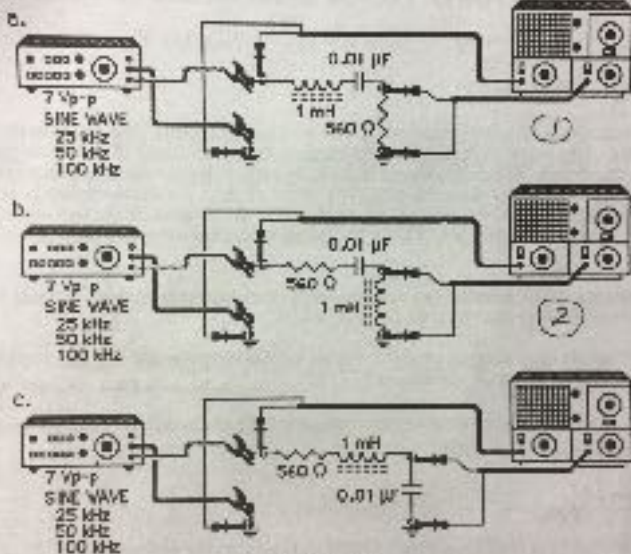


FIGURE 1

8

overpage. →

9. At what frequency was the resistor voltage the greatest? 50 kHz Explain why. Maximum power transfer, the R is all that exists
10. When the circuit is acting inductively, does the resistor voltage lead the source voltage? Yes Explain. V_s leads V_R when circuit behaves inductively develop V_{drop} across.

TABLE 2 $I_T \times V_s$ $I^2 R$ $I V$ $I \cdot V$ $I^2 R_{wr}$

	P_A	P_R	P_L	P_C	P_T	PF
3-26mA 25 kHz	3.05m 3.05mVA	5.95m 5.95mW	1.3mW	6.52mW	5.95mW	$\frac{5.95}{8.05} = 0.74$
4-38mA 50 kHz	10.8mVA	10.7mW	4.7mW	5.9mW	10.7mW	$\frac{10.7}{10.5} = PF=1$
3-76mA 100 kHz	9.28mVA	7.9mW	7mW	2.2mW	7.9mW	$\frac{7.9}{9.28} = 0.85$

PART TWO QUESTIONS

1. At which frequency is the power factor closest to 1 (100%)? 50 kHz
2. At which frequency is the real power closest to the apparent power? 50 kHz
3. In step 6, a second 0.01 μF capacitor was added to the circuit. What was the total capacitance of the two capacitors. $C_t = 0.01 \mu F + 0.01 \mu F = 0.02 \mu F$

4. Calculate the inductive reactance and the total capacitive reactance, using the total capacitance calculated above, as the circuit operated at 35 kHz. $X_L = (176 \Omega)$, $X_C = 227 \Omega$

Explain why the power delivered to the resistor increased when the second capacitor was added. I think they phased $X_C = X_L$ so cancellation of reactance.

6. What happened to the phase shift between the resistor voltage and the source voltage when the second capacitor was added? zero phase shift See my kb notes.
7. Explain how the power factor of a series RCL circuit that is acting inductively can be corrected. add more capacitance to balance the circuit current.
8. List three characteristics of a series RCL circuit whose power factor is 1 (100% efficient).
- $X_L = X_C$
 - $V_s = V_R$ with no phase shift
 - phase angle is zero.
 - at resonance fr

PART TWO: POWER AND POWER FACTOR IN SERIES RCL AC CIRCUITS

$$P_A = I_t \cdot E_s \quad P_R = I_t \cdot V_R \quad P_L = I_t \cdot V_L \quad P_C = I_t \cdot V_C$$

$$P_T = P_L + P_C \quad \text{PF} = P_R / P_A$$

In this part of the experiment, you will calculate the power at each frequency of each component in the RCL test circuit. You will also experimentally improve the power factor (PF) of your circuit while it is acting capacitively. Recall that power factor is the ratio of real power to apparent power. When multiplied by 100%, it expresses the efficiency of the circuit. An improvement in power factor, or efficiency, is obtained when changes are made to the circuit to cause the two reactances to be closer in value. The RCL circuit is 100% efficient when the inductive and capacitive reactances are equal.

1. Use the experimental data from Table 1 to calculate all of the power parameters in Table 2. Don't forget to label all values correctly (W, VA, VAR).

2. Connect your circuit once again as shown in Figure 1a. Set the generator frequency to 35 kHz, 7 V_{pp}. How is the circuit acting now? 30° phase shift

3. Measure and record the peak-to-peak resistor voltage and the phase shift between the resistor voltage and the source voltage ($\angle\theta$).

$$V_{R(P-P)} = \underline{2.1 \text{ V}_{RMS}} \quad \angle\theta = \underline{30^\circ} \quad I_T = \frac{2.1}{560}$$

4. Convert the peak-to-peak resistor voltage to RMS and calculate the resistor power (real power). 3.75 mA

$$V_R = \underline{2.1 \text{ V}_{RMS}} \quad P_R = V_R^2 / R = \underline{7.87 \text{ mW}}$$

5. List two things that can be done to correct, or improve, the power factor.

1. _____
2. _____

6. Place a second 0.01 μF capacitor in parallel with the one that is in your circuit.

7. Measure and record the peak-to-peak resistor voltage and the phase shift between the resistor voltage and the source voltage ($\angle\theta$).

$$V_{R(P-P)} = \underline{2.31 \text{ V}_{RMS}} \quad \angle\theta = \underline{-7^\circ}$$

$$PF = \frac{P_T}{P_A}$$

8. Convert the peak-to-peak resistor voltage to RMS and calculate the resistor power (real power).

$$V_R = \underline{2.31 \text{ V}_{RMS}} \quad P_R = V_R^2 / R = \underline{9.52 \text{ mW}}$$

$$I_T = \underline{4.1 \text{ mA}}$$

9. Remove power and answer all questions for Part Two.