

CLASS A LARGE SIGNAL

Bernabe P164

①

$$V_B = 3.134V$$


$$V_E = 2.408$$

$$V_C = 12.8V$$

$$I_{C(SAT)} = \frac{20}{300 + 15 + 85}$$

$$\begin{aligned} DC\ V_{CE(Q)} &= V_C - V_E + V_C \\ &= 12.8 - 2.408 \\ &= 10.392V \end{aligned}$$

$i_{c(sat)} 90\text{mA}$

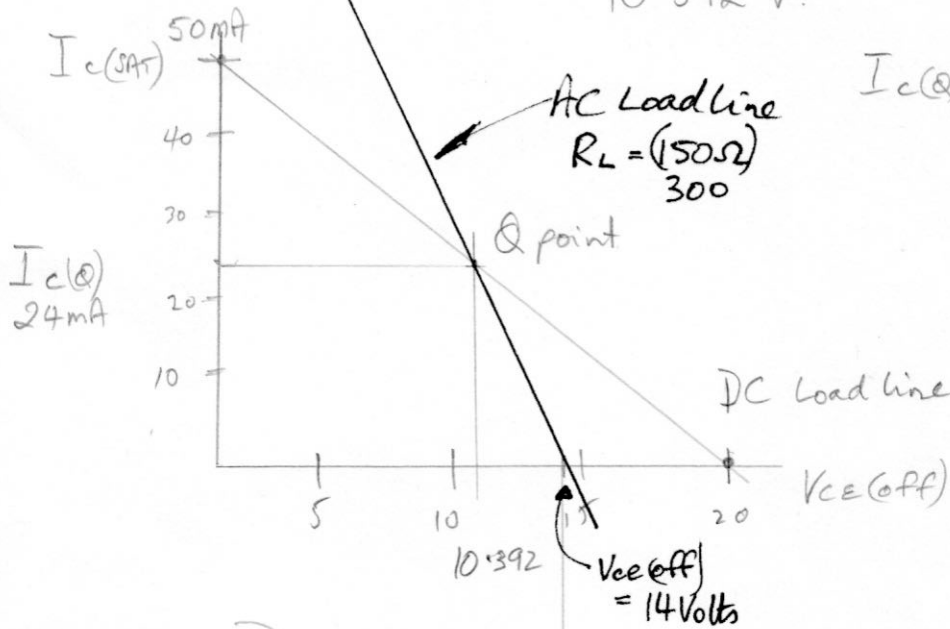

$$\begin{aligned} I_{C(Q)} &= \frac{2.408}{100} \\ &= 24\text{mA} \end{aligned}$$

$$\left. \begin{aligned} R_C &= 300\Omega \\ R_L &= 300\Omega \end{aligned} \right\} \therefore r_c = 150\Omega$$

$$\begin{aligned} i_{c(SAT)} &= I_{C(Q)} + \frac{V_{ce(Q)}}{r_c} \\ &= 24\text{mA} + \frac{10.4}{150} \\ &= 24\text{mA} + 69\text{mA} \\ &= 93\text{mA} \end{aligned}$$


$$\begin{aligned} V_{ce(off)} &= V_{ce(Q)} + I_{C(Q)} r_c \\ &= 10.4 + 24\text{mA} \times 150 \\ &= 14\text{Volts} \end{aligned}$$

Compliance

$$(14\text{Volts} - 10.4) \times 2 = 7.2\text{Volts pp}$$

measured on graph.

Use 2 equations to check. see over.

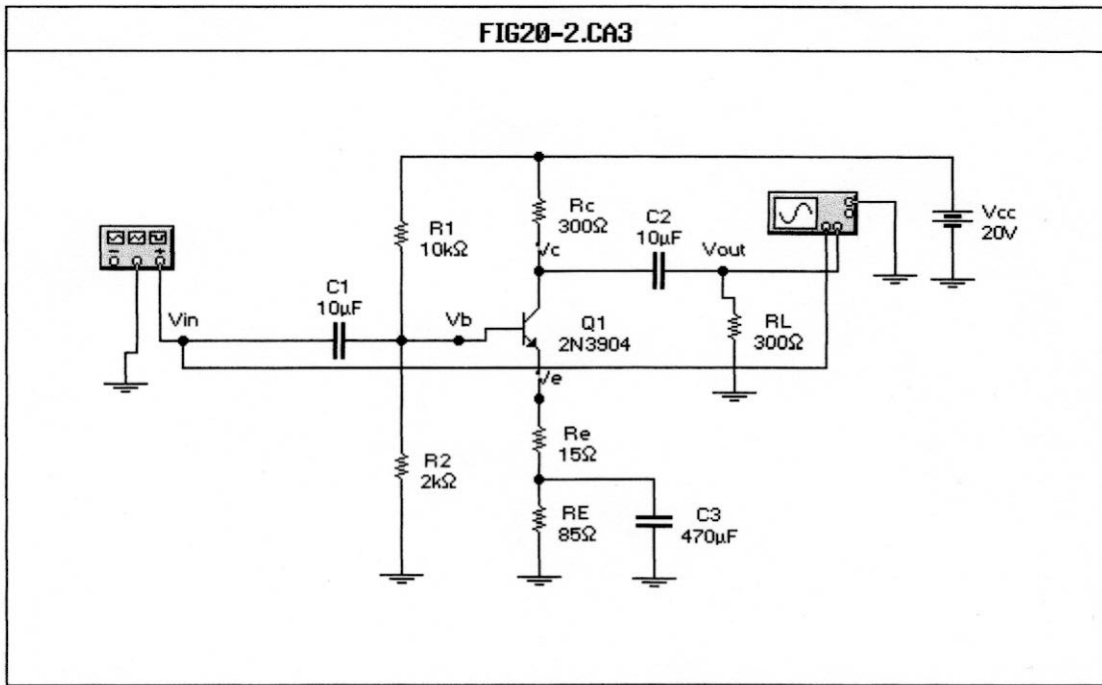

Compliance

Case # 1 = $2 \times I_{c(Q)} r_c$
 cutoff clipping
 $= 2 \times 24 \text{ mA} \times 150 \Omega$
 $= 7.2 \text{ Vpp}$

Case # 2 = $2 \times V_{ce(Q)}$
 saturation clipping
 $= 2 \times 10.4$
 $= 20.8$

← Smaller of the two.
 ≠ equal with graphical results.


Measured o/p.

440 mV_{pk} input to produce onset of distortion of positive peaks in o/p signal. $V_{opp} = 4.1 + 3.6 = 7.7 \text{ Vpp}$

Calculated A_v = $\frac{r_c}{r'_e + 15 \Omega}$ $\frac{25 \text{ mV}}{24 \text{ mA}}$
 $= \frac{r_c}{16 \Omega} = 9.4$ $(9.4 \times 440 \text{ mV} = 8.2 \text{ Vpp})$
 9.4 Very close.

Note the amp cannot provide any more o/p due to the limited swing provided by the AC load line position.

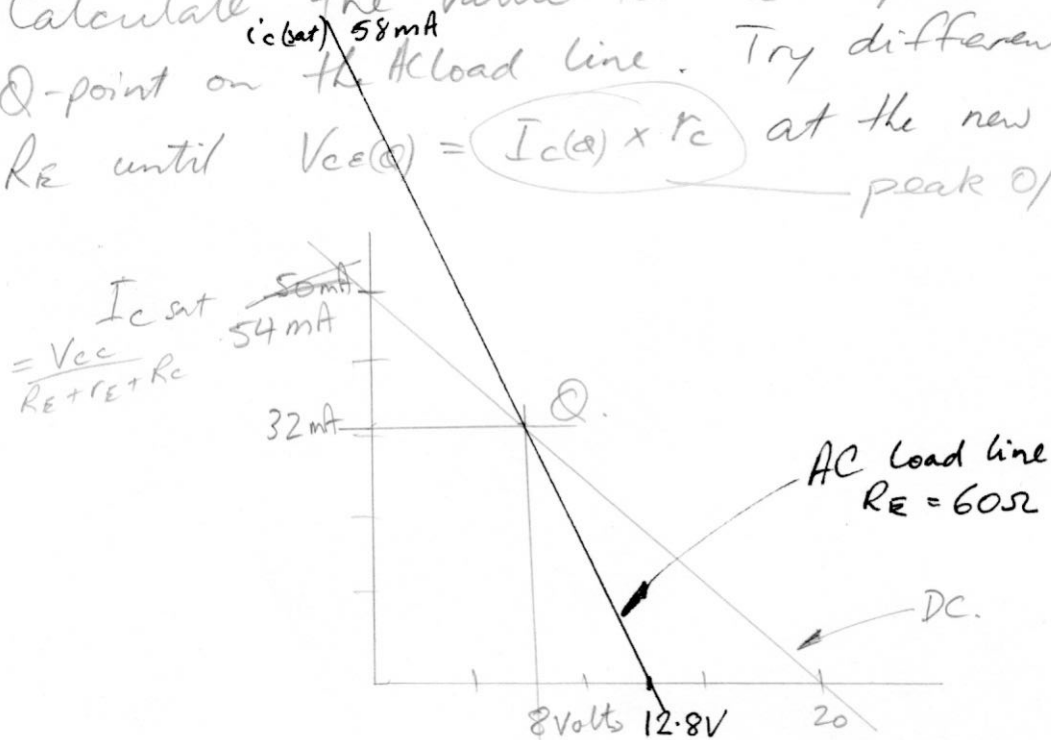Calculate the value for R_E required to center the Q-point on the AC load line. Try different values for R_E until $V_{CE(Q)} = I_{C(Q)} \times r_c$ at the new Q point. peak O/P voltage.



Case #1. $R_E = 60 \Omega$ $I_{C(Q)} = \frac{V_E}{R_E} = \frac{2.4}{60 + 15}$

$$V_{CE(Q)} = V_{CC} - I_{C(Q)}(R_E + r_E + R_c) = 32 \text{ mA}$$

$$= 8 \text{ Volts}$$

$$V_{CE(Q)} = V_{CE(Q)} + I_{C(Q)} r_c \quad i_c(\text{sat}) = I_{C(Q)} + \frac{V_{CE(Q)}}{r_c}$$

$$= 8 + 32 \text{ mA } 150 \Omega = 58 \text{ mA}$$

$$= 12.8 \text{ Volts}$$

Compliance = $(12.8 - 8) \times 2$ (from graph.)

$$= 9.6 \text{ V}_{PP} \rightarrow \text{ie } V_{PP} = 2 \times I_{C(Q)} r_c$$

Test $r_c \times I_{C(Q)} = V_{CE(Q)}$

$$4.8 = 8 \quad \text{no good.}$$

Case #2.

$$R_E = 50 \Omega$$

$$I_{C(Q)} = \frac{V_E}{R_E} = \frac{2.4}{50+15}$$

$$\doteq 37 \text{ mA}$$

$$V_{CE(Q)} = V_{CC} - I_{C(Q)} (R_E + r_E + R_C)$$

$$= 20 - (.037 \times 365)$$

$$= 6.5 \text{ V}$$

Test $r_C \times I_{C(Q)} = V_{CE(Q)}$

$$150 \times .037 = 5.5$$

$$\underline{\underline{5.5 \text{ Vs } 6.5}}$$

Case #3

$$R_E = 46 \Omega$$

$$I_{C(Q)} = \frac{V_E}{R_E} = \frac{2.4}{46+15}$$

$$\doteq 41 \text{ mA}$$

$$V_{CE(Q)} = V_{CC} - I_{C(Q)} (R_E + r_E + R_C)$$

$$20 - (.041 \times 359)$$

$$= 20 - 14.7$$

$$= 5.3$$


Test $r_C \times I_{C(Q)} = V_{CE(Q)} ?$

$$150 \times .041 =$$

$$\underline{\underline{6.15 = 5.3}}$$

gone the other way!

value must be 48Ω ✓

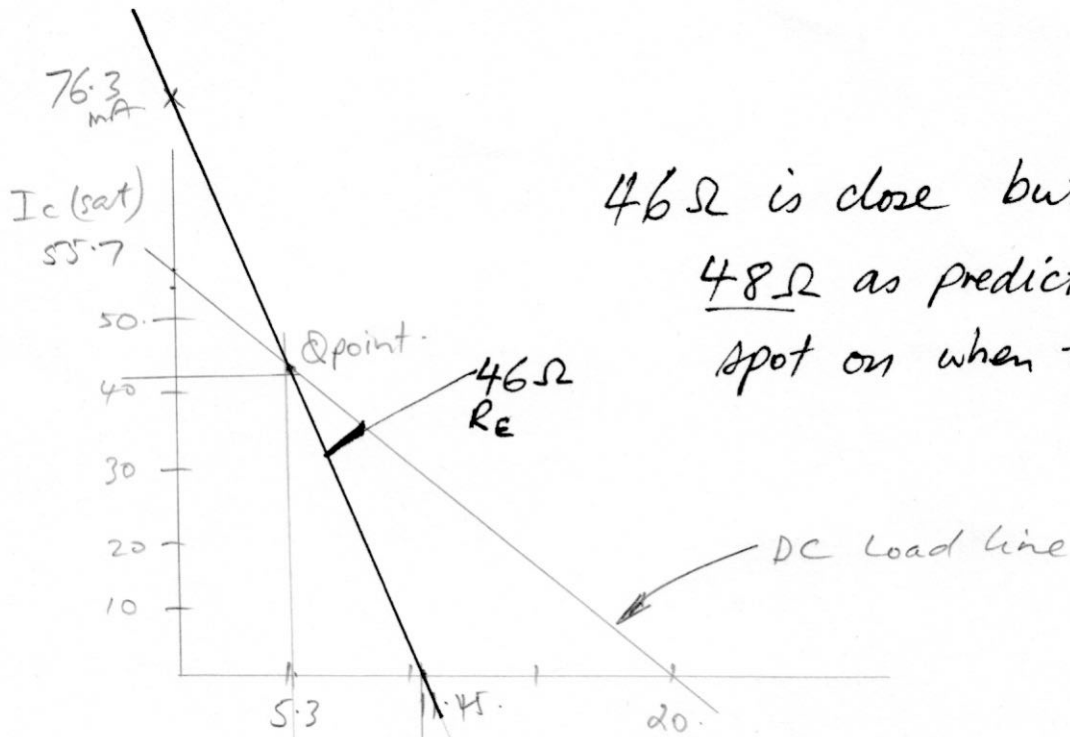

46Ω is close but
48Ω as predicted is
 spot on when tested in cct.

Case # 3.
 plotted

$$R_E = 46\Omega$$

$$V_{CE(Q)} = 5.3V$$

$$I_{C(sat)} = \frac{V_{CC}}{R_E + r_E + R_C}$$

$$I_{C(Q)} = 41mA$$

$$= \frac{20}{359}$$

$$= 55.7mA$$

$$V_{CE(off)} = V_{CE(Q)} + I_{C(Q)} R_C$$

$$= 5.3 + (41mA \times 150\Omega)$$

$$= 11.45V$$

$$I_{C(sat)} = I_{C(Q)} + \frac{V_{CE(Q)}}{r_c}$$

$$= 41mA + \frac{5.3}{150}$$

$$= 76.3mA$$

Compliance = $(11.45 - 5.3) \times 2$
 = $(12.3 V_{pp})$ BUT notice $V_{CE} = 0$ Volts
 is only 5.3 Volts away.

So $V_{pp} = 2 \times V_{CE(Q)} = 2 \times 5.3 = \boxed{10.6 \text{ Volts}}$
 not allowing for $V_{CE} < 1 \text{ volt!}$

P_s The input power to the amplifier:

$$I_{cc} = \left(\frac{V_{cc}}{R_1 + R_2} \right) + I_{c(Q)} \quad \text{Case 3.}$$

$$= 1.66 \text{ mA} + 41 \text{ mA}$$

$$= 42.66 \text{ mA.} \quad \text{So } P_s = V_{cc} \times I_{cc}$$

$$= 20 \times 42.66$$

$$= 850 \text{ mW.}$$

$$P_o = \frac{V_{pp}^2}{8R_L} \doteq \frac{10.6^2}{8 \times 300}$$

$$= 46 \text{ mW.}$$

efficiency $\eta = \frac{P_o}{P_s}$

$$= \frac{46}{850}$$

$$= 5.4\%$$