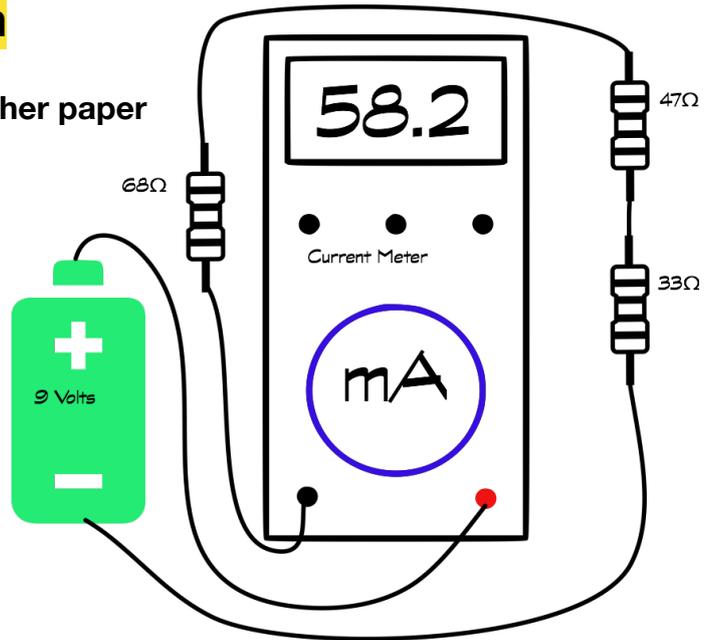


Homework for Week 2, DC Circuits - Hand in at 8am

Question 1 show all workings on another paper or preferably in your exercise book.

Examine the adjacent circuit.

Answer the questions




- What is the calculated value of current in this circuit?
- Is there a difference in the calculated current and the measured current and why or why not?
- What is the total resistance of all 3 resistors?
- What voltage will you measure across 68Ω ? with current meter in circuit.
- What voltage will you measure across 47Ω ? with current meter in circuit.
- What voltage will you measure across 33Ω ? with current meter in circuit
- Do the 3 voltages add to 9 Volts? Show addition
- If there is a difference explain why
- If you think some voltage is dropped across the meter, explain how this can be so
- If in (i) you answered yes, what voltage
- If in (i) you answered yes, what calculated resistance must the meter have?
- Removing the current meter from the circuit, redraw circuit and show all new voltage values across 33Ω , 68Ω , 47Ω .
- What would a suitable internal resistance be for the current meter? Why? Show example with maths.
- State what Kirchhoffs Voltage Law is

Overpage...

Question 2 show all workings

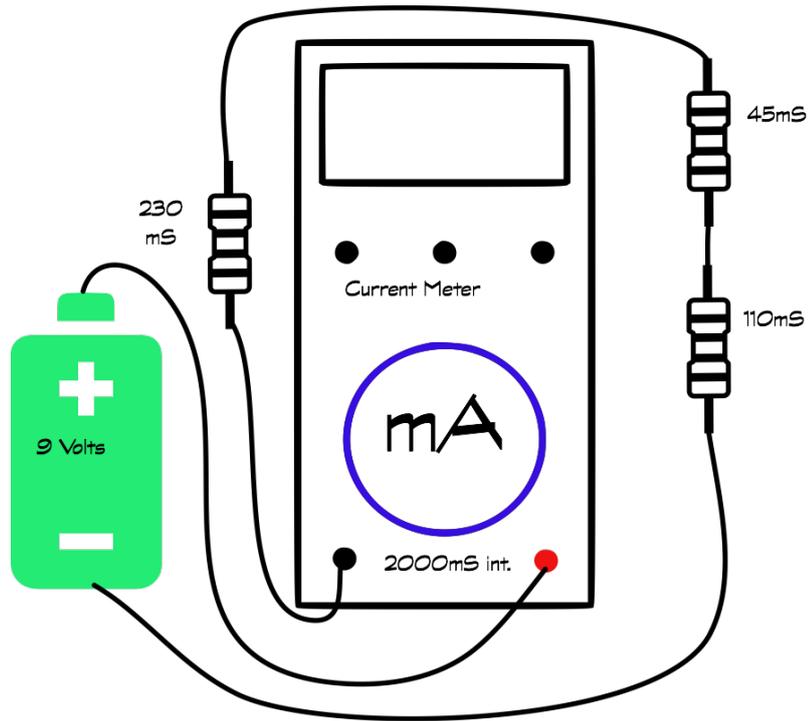- a) Calculate the value of each resistor in Ω
- b) What is the total resistance of the 3 external resistors?
- c) Calculate the resistance value of the wire conductors
- d) Calculate the total resistance of the circuit.
- e) What should be the circuit current then?
- f) Does the current meter have any resistance?



Wires are all 45S/Metre conductance and have a total wire length of 33cm.

- g) Did you include the current meter $R_{int.}$ in your resistance calculations?
- h) Determine with maths the proper current flow in the circuit without the meter connected in series.
- i) Determine the proper voltage drop across each resistor without the current meter connected in series with the circuit.
- j) Did you include the wire resistance in your calculations for (g) & (h)?
- k) Including the wires in your calculations, what voltage will be lost in the circuit due to the conducting wires? (excluding meter)
- l) Including the meter R , wire R , show what the measured values of current and voltage will be in this circuit.
- m) If the wires were 3 Metres long, what extra voltage will be lost across the wires in the circuit?