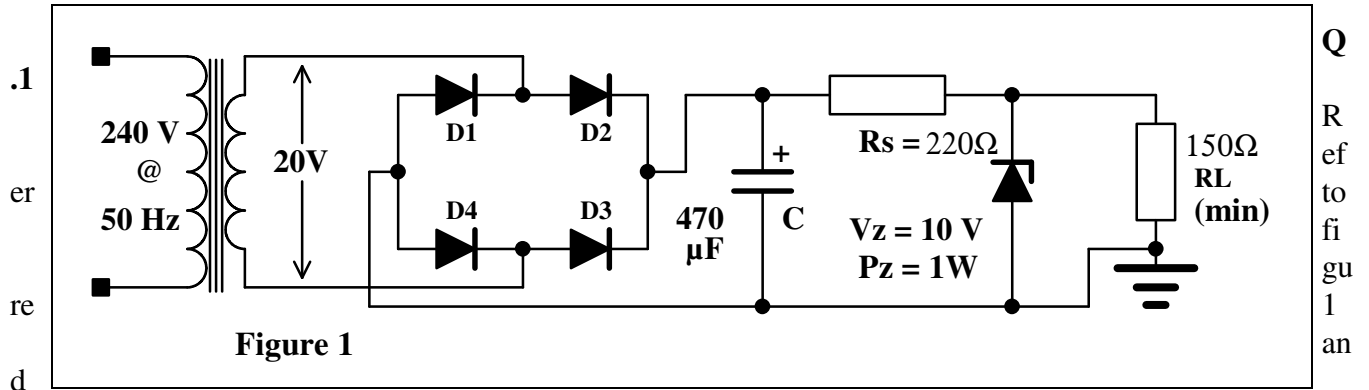


Power Supply and Zener Regulator Problems



complete the following

i) $I_z(\max) =$ _____


ii) $I_z(\min) =$ _____

iii) $I_L(\max) =$ _____

iv) $V_{(\text{ripple}) \text{ p-p}} =$ _____

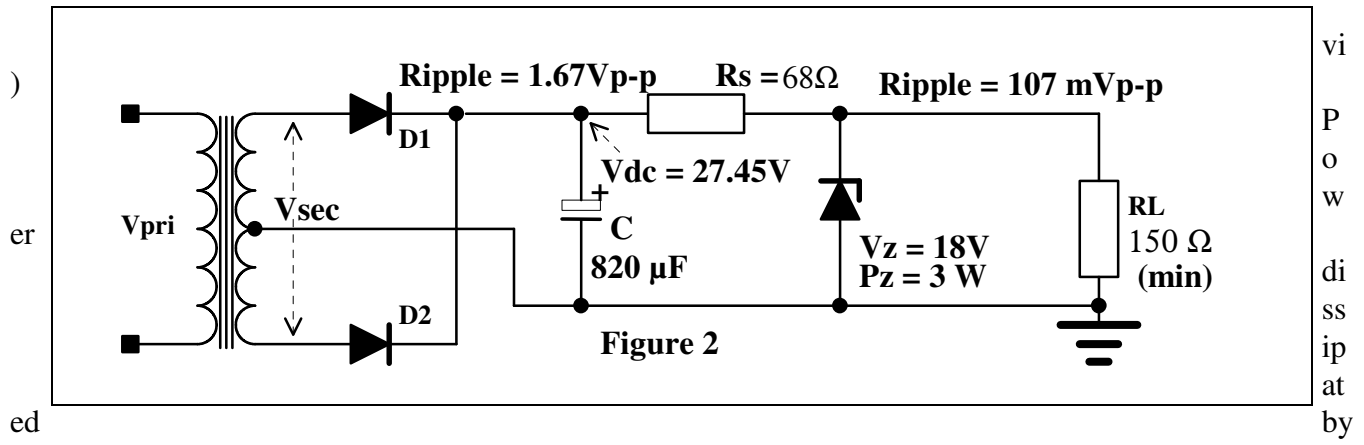v) $V_{\text{dc}}(\text{across } C) =$ _____

NE178 - Dc Power Supplies - Lesson 6 - Theory



ed
Rs = _____

vi
P
o
w
er
d
i
s
s
i
p
a
t
i
o
n

vii) Current through the zener if R_L is open circuit = _____

viii) Voltage across R_L if it was a value of 100Ω = _____


Q.2 Refer to the circuit of figure 2 and complete the following.

i) I_L (max) = _____

ii) I_{R_s} = _____

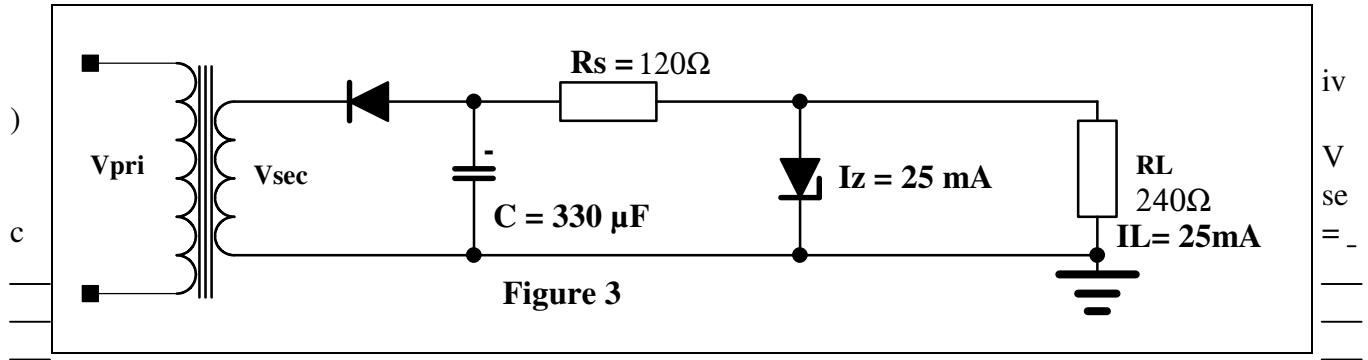iii) P_{R_s} = _____

NE178 - Dc Power Supplies - Lesson 6 - Theory



v) The ripple reduction factor of the regulator circuit = _____

vi) the output voltage if the zener went open circuit = _____

vii) The regulation percentage of the power supply if the voltage across the zener went to 18.7 V with R_L open circuit.

Q.3 Refer to figure 3 and complete the following

NE178 - Dc Power Supplies - Lesson 6 - Theory

i) Value of $V_z =$ _____

ii) Select a minimum available power rating for the zener. = _____

iii) Ripple voltage across C = _____

iv) Voltage drop across $R_s =$ _____

v) Value of the transformer secondary voltage = _____

vi) The approximate voltage supplied to the load if the zener diode became open circuit = _

vii) The current through the zener if R_L become open circuit. = _____

Equations

Transformers

$$\frac{N_{pri}}{N_{sec}} = \frac{V_{pri}}{V_{sec}} = \frac{I_{sec}}{I_{pri}}$$

$$V_{sec\ pk} = V_{sec} \times \sqrt{2}$$

NE178 - Dc Power Supplies - Lesson 6 - Theory

Rectifier Systems (Unfiltered)

$$V_{RL(pk)} = V_{sec(pk)} - V_d$$

$V_d = 0.7$ V for half wave and full wave center tapped transformer. 1.4 V for bridge circuit.

$$V_{dc} = V_{RL(pk)} \times 0.318$$

For half wave circuits.

$$V_{dc} = V_{RL(pk)} \times 0.637$$

For full wave circuits

The above rectifiers are not used for dc power supplies used in electronic equipment but may be used for battery charging and power control (motor speed, heating electro-plating etc)

Rectifier Systems (Filtered)

$$V_{RL(pk)} = V_{sec(pk)} - V_d$$

$V_d =$ as for above

$$V_{dc} = V_{RL(pk)} - \frac{V_{ripple-p-p}}{2}$$

For **ALL** filtered supplies

$$V_{ripple-p-p} = \frac{I_{dc} \times t}{C}$$

Where C = value of the filter capacitor
t = period of ripple frequency ($t = 1/f$)

Zener Regulation

$$P_Z = I_{Z(max)} \times V_Z$$

Transpose to find $I_{Z(max)}$

$$I_{Z(min)} = I_{Z(max)} \times 0.1$$

Value ensures that the zener is within the voltage regulation range.

$$I_{R_s} = I_Z + I_L$$

Transpose for I_Z once I_L is determined.

$$I_{R_s} = \frac{V_{dc} - V_Z}{R_s}$$

Transpose for R_s if I_{R_s} is known.

$$\text{Ripple reduction factor} = \frac{V_{ripple(in)}}{V_{ripple(out)}}$$